

DDCO ASSIGNMENT 3


31-08-23

GAUTAM V HANCHINAL

PES1UG22CS215

SECTION D

1) FULL ADDER:

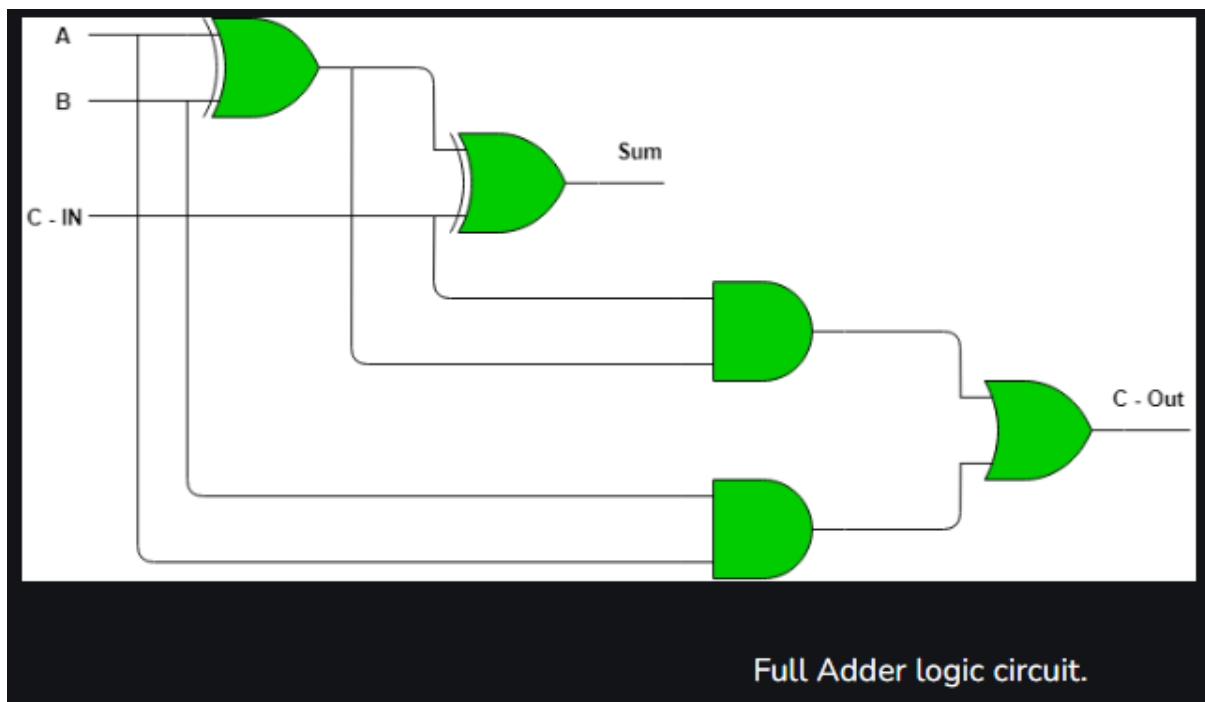

SOURCE : GEEKforGEEKS

Main Code:

```
module fulladder(input wire a,b,c,output wire sum,cout);
wire [4:0] t;

and a1(t[1],a,b);
and a2(t[2],a,c);
and a3(t[3],b,c);
or o1(t[4],t[1],t[2]);
or o2(cout,t[3],t[4]);
xor x1(t[0],a,b);
xor x2(sum,t[0],c);
endmodule
```

Test Bench:

```
fulladder_tb.v
File Edit View

module fulladd_tb;
    reg a, b, c;
    wire s, y;
    fulladd add1 (.a(a), .b(b), .c(c), .sum(s), .cout(y));

    initial begin
        $dumpfile("fulladd_test.vcd");
        $dumpvars(0, fulladd_tb);
    end

    initial begin
        $monitor($time, "a=%b, b=%b, c=%b, sum=%b, carry=%b", a, b, c, s, y);
        a = 1'b0; b = 1'b0; c = 1'b0;
        #5 a = 1'b0; b = 1'b0; c = 1'b1;
        #5 a = 1'b0; b = 1'b1; c = 1'b0;
        #5 a = 1'b0; b = 1'b1; c = 1'b1;
        #5 a = 1'b1; b = 1'b0; c = 1'b0;
        #5 a = 1'b1; b = 1'b0; c = 1'b1;
        #5 a = 1'b1; b = 1'b1; c = 1'b0;
        #5 a = 1'b1; b = 1'b1; c = 1'b1;
        $finish;
    end
endmodule
```


VVP Output:

```
Command Prompt - gtkwave
C:\Users\aimem\OneDrive\Desktop\assignment ddco\assignment 3>iverilog -o test1 fulladder.v.txt fulladder_tb.v.txt
C:\Users\aimem\OneDrive\Desktop\assignment ddco\assignment 3>vvp test1
VCD info: dumpfile fulladd_test.vcd opened for output.
      0a=0, b=0, c=0, sum=0, carry=0
      5a=0, b=0, c=1, sum=1, carry=0
     10a=0, b=1, c=0, sum=1, carry=0
     15a=0, b=1, c=1, sum=0, carry=1
     20a=1, b=0, c=0, sum=1, carry=0
     25a=1, b=0, c=1, sum=0, carry=1
     30a=1, b=1, c=0, sum=0, carry=1
     35a=1, b=1, c=1, sum=1, carry=1

C:\Users\aimem\OneDrive\Desktop\assignment ddco\assignment 3>gtkwave fulladd_test.vcd
GTKWave Analyzer v3.3.48 (w)1999-2013 BSI

[0] start time.
[35] end time.
|
```

GTKWAVE output:

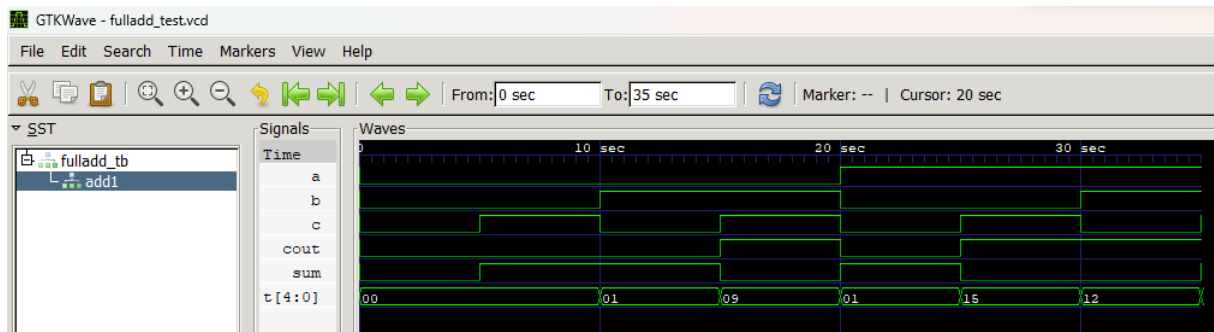

Truth Table:

Inputs			Outputs	
A	B	C – IN	Sum	C - Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


SOURCE : GEEKforGEEKS

2) 2:1 MUX

The logical expression of the term Y is as follows:

$$Y = S_0' \cdot A_0 + S_0 \cdot A_1$$

 Logical circuit of the above expression is given below:



SOURCE: javatpoint.com/multiplexer-digital-electronics

Main Code:

```
module mux2 (input wire a, b, x, output wire o);
assign o = (a & (~x))+(b & x);
endmodule
```

Test Bench:

```
2isto1MUX.v 2isto1MUX_tb.v X
File Edit View

module testbench;

reg A,B,S;
wire X;

initial
begin
$dumpfile("MUX2isto1_test.vcd");
$dumppvars(0,testbench);
end

mux2 newMUX(.a(A), .b(B), .x(S), .o(X));

initial
begin
S = 1'b0;A = 1'b0;B = 1'b0;
#5 S = 1'b0;A = 1'b0;B = 1'b1;
#5 S = 1'b0;A = 1'b1;B = 1'b0;
#5 S = 1'b0;A = 1'b1;B = 1'b1;
#5 S = 1'b1;A = 1'b0;B = 1'b0;
#5 S = 1'b1;A = 1'b0;B = 1'b1;
#5 S = 1'b1;A = 1'b1;B = 1'b0;
#5 S=1'b1;A = 1'b1;B = 1'b1;
end

initial
begin
$monitor($time, "S=%b, A=%b, B=%b, X=%b", S,A,B,X);
S = 1'b0;A = 1'b0;B = 1'b0;
#5 S = 1'b0;A = 1'b0;B = 1'b1;
#5 S = 1'b0;A = 1'b1;B = 1'b0;
#5 S = 1'b0;A = 1'b1;B = 1'b1;
#5 S = 1'b1;A = 1'b0;B = 1'b0;
#5 S = 1'b1;A = 1'b0;B = 1'b1;
#5 S = 1'b1;A = 1'b1;B = 1'b0;
#5 S = 1'b1;A = 1'b1;B = 1'b1;
end

endmodule
```

VVP output:

```
Command Prompt - gtkwave
Microsoft Windows [Version 10.0.22621.2134]
(c) Microsoft Corporation. All rights reserved.

C:\Users\aimem\OneDrive\Desktop\assignment ddco\assignment 3\2isto1 MUX>iverilog -o test1 2isto1MUX.v.txt 2isto1MUX_tb.v.txt


C:\Users\aimem\OneDrive\Desktop\assignment ddco\assignment 3\2isto1 MUX>vvp test1
VCD info: dumpfile MUX2isto1_test.vcd opened for output.
      0S=0, A=0, B=0, X=0
      5S=0, A=0, B=1, X=0
     10S=0, A=1, B=0, X=1
     15S=0, A=1, B=1, X=1
     20S=1, A=0, B=0, X=0
     25S=1, A=0, B=1, X=1
     30S=1, A=1, B=0, X=0
     35S=1, A=1, B=1, X=1

C:\Users\aimem\OneDrive\Desktop\assignment ddco\assignment 3\2isto1 MUX>gtkwave MUX2isto1_test.vcd

GTKWave Analyzer v3.3.48 (w)1999-2013 BSI

[0] start time.
[35] end time.
```

GTKWAVE output:

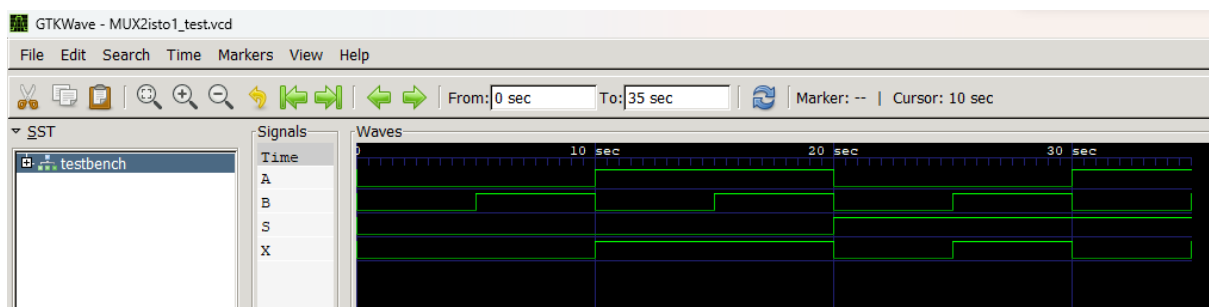

Truth Table:

$INPUT(s)$	$OUTPUT$
S_o	X
0	A
1	B