

DDCO ASSIGNMENT

3rd Semester

D section

25-10-2023

Gautam Hanchinal

PES1UG22CS215

DDCO

1. CODES

```
module invert (input wire i, output wire o);
    assign o = !i;
endmodule

module and2 (input wire i0, i1, output wire o);
    assign o = i0 & i1;
endmodule

module or2 (input wire i0, i1, output wire o);
    assign o = i0 | i1;
endmodule

module xor2 (input wire i0, i1, output wire o);
    assign o = i0 ^ i1;
endmodule

module nand2 (input wire i0, i1, output wire o);
    wire t;
    and2 and2_0 (i0, i1, t);
    invert invert_0 (t, o);
endmodule

module nor2 (input wire i0, i1, output wire o);
    wire t;
    or2 or2_0 (i0, i1, t);
    invert invert_0 (t, o);
endmodule

module xnor2 (input wire i0, i1, output wire o);
    wire t;
    xor2 xor2_0 (i0, i1, t);
    invert invert_0 (t, o);
endmodule

module and3 (input wire i0, i1, i2, output wire o);
    wire t;
    and2 and2_0 (i0, i1, t);
    and2 and2_1 (i2, t, o);
endmodule

module or3 (input wire i0, i1, i2, output wire o);
    wire t;
    or2 or2_0 (i0, i1, t);
    or2 or2_1 (i2, t, o);
endmodule
```

```

|
module nor3 (input wire i0, i1, i2, output wire o);
    wire t;
    or2 or2_0 (i0, i1, t);
    nor2 nor2_0 (i2, t, o);
endmodule

module nand3 (input wire i0, i1, i2, output wire o);
    wire t;
    and2 and2_0 (i0, i1, t);
    nand2 nand2_1 (i2, t, o);
endmodule

module xor3 (input wire i0, i1, i2, output wire o);
    wire t;
    xor2 xor2_0 (i0, i1, t);
    xor2 xor2_1 (i2, t, o);
endmodule

module xnor3 (input wire i0, i1, i2, output wire o);
    wire t;
    xor2 xor2_0 (i0, i1, t);
    xnor2 xnor2_0 (i2, t, o);
endmodule

module mux2 (input wire i0, i1, j, output wire o);
    assign o = (j==0)?i0:i1;
endmodule

module mux4 (input wire [0:3] i, input wire j1, j0, output wire o);
    wire t0, t1;
    mux2 mux2_0 (i[0], i[1], j1, t0);
    mux2 mux2_1 (i[2], i[3], j1, t1);
    mux2 mux2_2 (t0, t1, j0, o);
endmodule

module mux8 (input wire [0:7] i, input wire j2, j1, j0, output wire o);
    wire t0, t1;
    mux4 mux4_0 (i[0:3], j2, j1, t0);
    mux4 mux4_1 (i[4:7], j2, j1, t1);
    mux2 mux2_0 (t0, t1, j0, o);
endmodule

```

```

module demux2 (input wire i, j, output wire o0, o1);
    assign o0 = (j==0)?i:1'b0;
    assign o1 = (j==1)?i:1'b0;
endmodule

module demux4 (input wire i, j1, j0, output wire [0:3] o);
    wire t0, t1;
    demux2 demux2_0 (i, j1, t0, t1);
    demux2 demux2_1 (t0, j0, o[0], o[1]);
    demux2 demux2_2 (t1, j0, o[2], o[3]);
endmodule

module demux8 (input wire i, j2, j1, j0, output wire [0:7] o);
    wire t0, t1;
    demux2 demux2_0 (i, j2, t0, t1);
    demux4 demux4_0 (t0, j1, j0, o[0:3]);
    demux4 demux4_1 (t1, j1, j0, o[4:7]);
endmodule

module df (input wire clk, in, output wire out);
    reg df_out;
    always@(posedge clk) df_out <= in;
    assign out = df_out;
endmodule

module dfr (input wire clk, reset, in, output wire out);
    wire reset_, df_in;
    invert invert_0 (reset, reset_);
    and2 and2_0 (in, reset_, df_in);
    df df_0 (clk, df_in, out);
endmodule

module dfr1 (input wire clk, reset, load, in, output wire out);
    wire _in;
    mux2 mux2_0(out, in, load, _in);
    dfr dfr_1(clk, reset, _in, out);
endmodule

```

2. TEST BENCH CODE

```
`timescale 1 ns / 100 ps
`define TESTVECS 5

module tb;
    reg clk, reset, inc, add, sub;
    reg [15:0] offset;
    wire [15:0] pc;
    reg [18:0] test_vecs [0:(`TESTVECS-1)];
    integer i;
    initial begin $dumpfile("tb_pc.vcd"); $dumpvars(0,tb); end
    initial begin reset = 1'b1; #12.5 reset = 1'b0; end
    initial clk = 1'b0; always #5 clk =~ clk;
    initial begin
        test_vecs[0][18] = 1'b1; test_vecs[0][17] = 1'b0; test_vecs[0][16] = 1'b0;
        test_vecs[0][15:0] = 15'hxx;
        test_vecs[1][18] = 1'b0; test_vecs[1][17] = 1'b1; test_vecs[1][16] = 1'b0;
        test_vecs[1][15:0] = 15'ha5;
        test_vecs[2][18] = 1'b0; test_vecs[2][17] = 1'b0; test_vecs[2][16] = 1'b0;
        test_vecs[2][15:0] = 15'hxx;
        test_vecs[3][18] = 1'b1; test_vecs[3][17] = 1'b0; test_vecs[3][16] = 1'b0;
        test_vecs[3][15:0] = 15'hxx;
        test_vecs[4][18] = 1'b0; test_vecs[4][17] = 1'b0; test_vecs[4][16] = 1'b1;
        test_vecs[4][15:0] = 15'h14;
    end
    end
    initial {inc, add, sub, offset} = 0;
    pc pc_0 (clk, reset, inc, add, sub, offset, pc);
    initial begin
        #6 for(i=0;i<`TESTVECS;i=i+1)
            begin #10 {inc, add, sub, offset}=test_vecs[i]; end
        #100 $finish;
    end
    end
    always@(reset or inc or add or sub )
    $monitor("At time = %t, Reset= %b,inc=%b, add=%b,sub = %b,pc =%h ", $time,reset,inc,add,sub,pc);

endmodule
```

3. MAIN FILE

```
module fa (input wire i0, i1, cin, output wire sum, cout);
  wire t0, t1, t2;
  xor3 _i0 (i0, i1, cin, sum);
  and2 _i1 (i0, i1, t0);
  and2 _i2 (i1, cin, t1);
  and2 _i3 (cin, i0, t2);
  or3 _i4 (t0, t1, t2, cout);
endmodule

module addsub (input wire addsub, i0, i1, cin, output wire sumdiff, cout);
  wire t;
  fa _i0 (i0, t, cin, sumdiff, cout);
  xor2 _i1 (i1, addsub, t);
endmodule

module pc_slice (input wire clk, reset, cin, load, inc, sub, offset, output wire cout, pc);
  wire in, inc_;
  invert invert_0 (inc, inc_);
  and2 and2_0 (offset, inc_, t);
  addsub addsub_0 (sub, pc, t, cin, in, cout);
  dfrl dfrl_0 (clk, reset, load, in, pc);
endmodule

module pc_slice0 (input wire clk, reset, cin, load, inc, sub, offset, output wire cout, pc);
  wire in;
  or2 or2_0 (offset, inc, t);
  addsub addsub_0 (sub, pc, t, cin, in, cout);
  dfrl dfrl_0 (clk, reset, load, in, pc);
endmodule

module pc (input wire clk, reset, inc, add, sub, input wire [15:0] offset, output wire [15:0] pc);
  input wire load;
  input wire [15:0] c;
  or3 or3_0 (inc, add, sub, load);
  pc_slice0 pc_slice_0 (clk, reset, sub, load, inc, sub, offset[0], c[0], pc[0]);
  pc_slice pc_slice_1 (clk, reset, c[0], load, inc, sub, offset[1], c[1], pc[1]);
  pc_slice pc_slice_2 (clk, reset, c[1], load, inc, sub, offset[2], c[2], pc[2]);
  pc_slice pc_slice_3 (clk, reset, c[2], load, inc, sub, offset[3], c[3], pc[3]);
  pc_slice pc_slice_4 (clk, reset, c[3], load, inc, sub, offset[4], c[4], pc[4]);
  pc_slice pc_slice_5 (clk, reset, c[4], load, inc, sub, offset[5], c[5], pc[5]);
  pc_slice pc_slice_6 (clk, reset, c[5], load, inc, sub, offset[6], c[6], pc[6]);
  pc_slice pc_slice_7 (clk, reset, c[6], load, inc, sub, offset[7], c[7], pc[7]);
  pc_slice pc_slice_8 (clk, reset, c[7], load, inc, sub, offset[8], c[8], pc[8]);
  pc_slice pc_slice_9 (clk, reset, c[8], load, inc, sub, offset[9], c[9], pc[9]);
  pc_slice pc_slice_10 (clk, reset, c[9], load, inc, sub, offset[10], c[10], pc[10]);
  pc_slice pc_slice_11 (clk, reset, c[10], load, inc, sub, offset[11], c[11], pc[11]);
  pc_slice pc_slice_12 (clk, reset, c[11], load, inc, sub, offset[12], c[12], pc[12]);
  pc_slice pc_slice_13 (clk, reset, c[12], load, inc, sub, offset[13], c[13], pc[13]);
  pc_slice pc_slice_14 (clk, reset, c[13], load, inc, sub, offset[14], c[14], pc[14]);
  pc_slice pc_slice_15 (clk, reset, c[14], load, inc, sub, offset[15], c[15], pc[15]);
endmodule
```

4. VVP TEST SCREENSHOT

```
C:\iverilog\bin>iverilog -o test1 lib.v pc.v tb_pc.v

C:\iverilog\bin>vvp test1
VCD info: dumpfile tb_pc.vcd opened for output.
At time =          0, Reset= 1,inc=0, add=0,sub = 0,pc =xxxx
At time =         50, Reset= 1,inc=0, add=0,sub = 0,pc =0000
At time =        130, Reset= 0,inc=0, add=0,sub = 0,pc =0000
At time =        160, Reset= 0,inc=1, add=0,sub = 0,pc =0000
At time =        250, Reset= 0,inc=1, add=0,sub = 0,pc =0001
At time =        260, Reset= 0,inc=0, add=1,sub = 0,pc =0001
At time =        350, Reset= 0,inc=0, add=1,sub = 0,pc =00a6
At time =        360, Reset= 0,inc=0, add=0,sub = 0,pc =00a6
At time =        460, Reset= 0,inc=1, add=0,sub = 0,pc =00a6
At time =        550, Reset= 0,inc=1, add=0,sub = 0,pc =00a7
At time =        560, Reset= 0,inc=0, add=0,sub = 1,pc =00a7
At time =        650, Reset= 0,inc=0, add=0,sub = 1,pc =0093
At time =        750, Reset= 0,inc=0, add=0,sub = 1,pc =007f
At time =        850, Reset= 0,inc=0, add=0,sub = 1,pc =006b
At time =        950, Reset= 0,inc=0, add=0,sub = 1,pc =0057
At time =       1050, Reset= 0,inc=0, add=0,sub = 1,pc =0043
At time =       1150, Reset= 0,inc=0, add=0,sub = 1,pc =002f
At time =       1250, Reset= 0,inc=0, add=0,sub = 1,pc =001b
At time =       1350, Reset= 0,inc=0, add=0,sub = 1,pc =0007
At time =       1450, Reset= 0,inc=0, add=0,sub = 1,pc =fff3
At time =       1550, Reset= 0,inc=0, add=0,sub = 1,pc =ffdf

C:\iverilog\bin>gtkwave tb_pc.vcd

GTKWave Analyzer v3.3.48 (w)1999-2013 BSI

[0] start time.
[156000] end time.
|
```

5. GTKWAVE SCREENSHOT

